

18-100 Introduction to Electrical and Computer Engineering

Lecture 09

Boolean Logic, Logic Gates, and Latches


Learning Objectives for This Lecture

- ***What is Boolean logic and what are logic gates.***
- ***How to use logic gates to build logic functions.***
- ***How computer uses binary numbers to control “things”.***
- ***How computer uses logic gates to do “computation”.***
- ***Latches and maintaining state***



A Simple Truth of “1” and “0”

Each transistor only controls a “1” and a “0”, however,

 8,500,000,000 Transistors can carry out very complex functions!



Binary Logic:


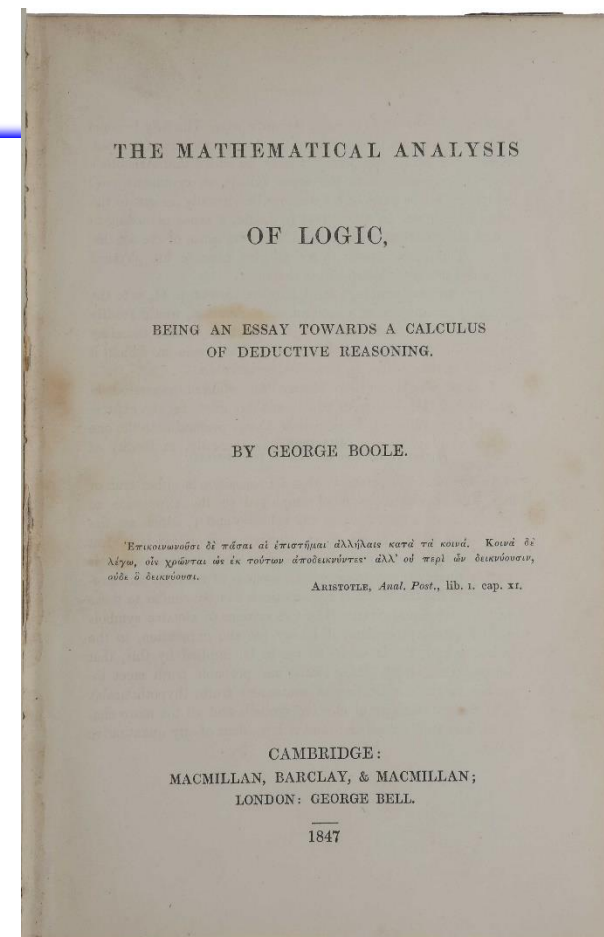
 


“True” = “1”

“False” = “0”

Binary bit operation: Simplest decision making






NOT Gate: Inverter

   

Truth Table $P = \bar{A}$

| Input | Output |
|-------|--------|
| 1 | 0 |
| 0 | 1 |

AND Gate

     


Truth Table

$$P = A \cdot B$$


| Input A | Input B | Output P |
|---------|---------|----------|
| 0 | 0 | 0 |
| 1 | 0 | 0 |
| 0 | 1 | 0 |
| 1 | 1 | 1 |

$$\left\{ \begin{array}{l} 0 \cdot 0 = 0 \\ 1 \cdot 0 = 0 \\ 0 \cdot 1 = 0 \\ 1 \cdot 1 = 1 \end{array} \right.$$

 
Using Logic Gates to Control Action: The Use of "1" and "0"



 
Using Logic Gates to Control Action: The Use of "1" and "0"



 
Using Logic Gates to Control Action: The Use of "1" and "0"



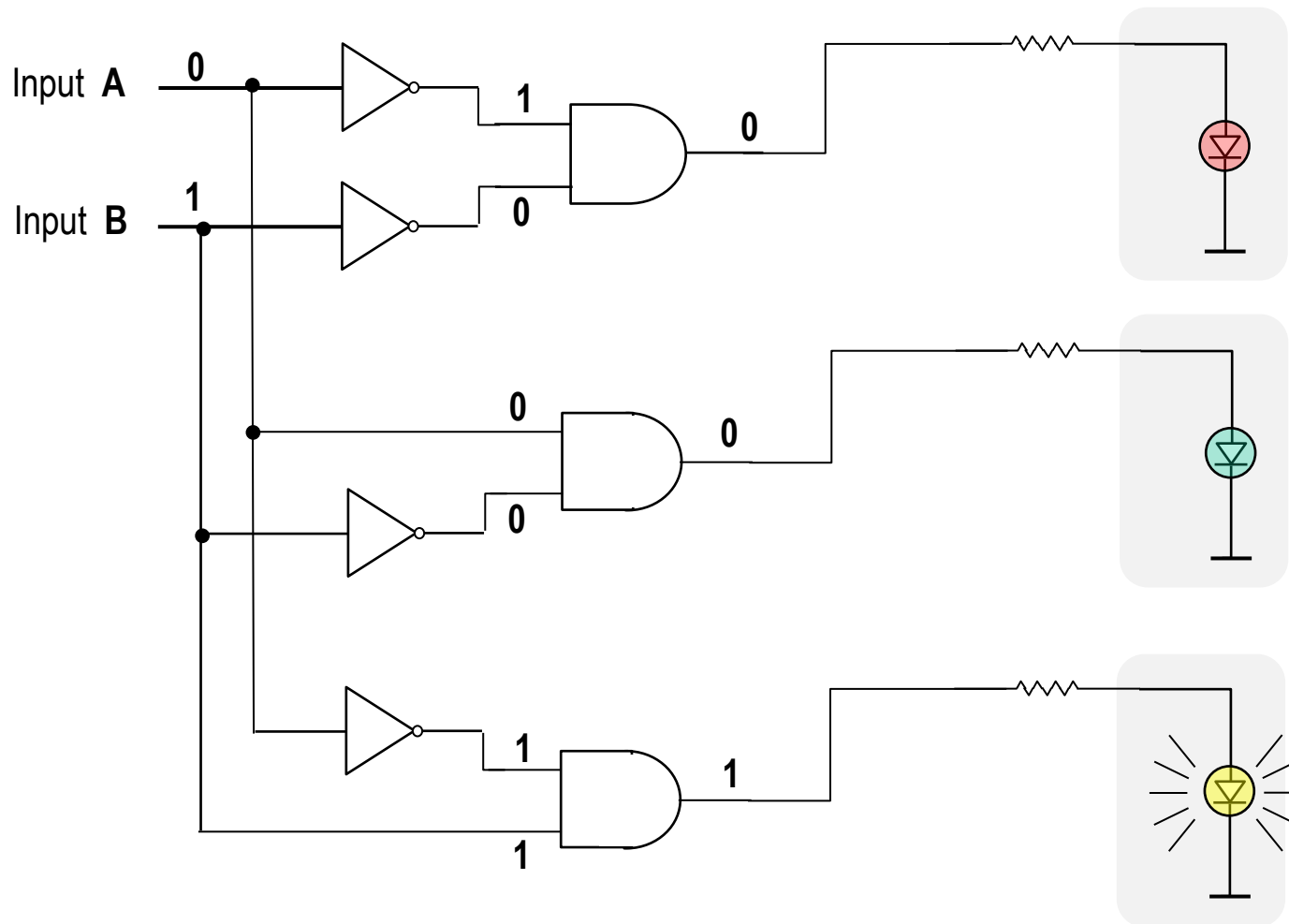Using Logic Gates to Control Action: The Use of “1” and “0”



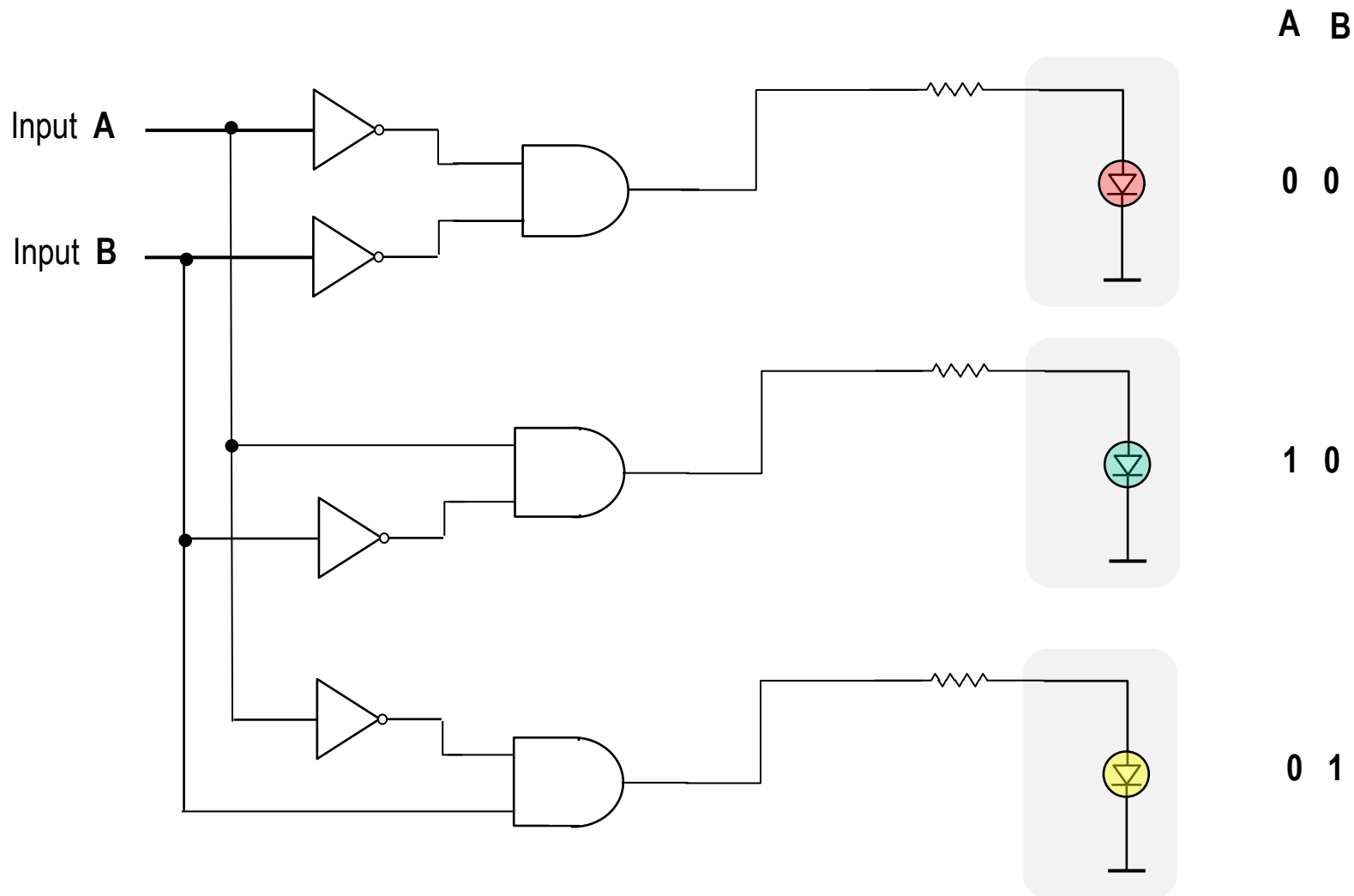
Using Logic Gates to Control Action: The Use of "1" and "0"



n-bit Input Controlling/Selecting 2^n Different Actions

A n -bit number has 2^n different values: Can be used to control 2^n different actions!

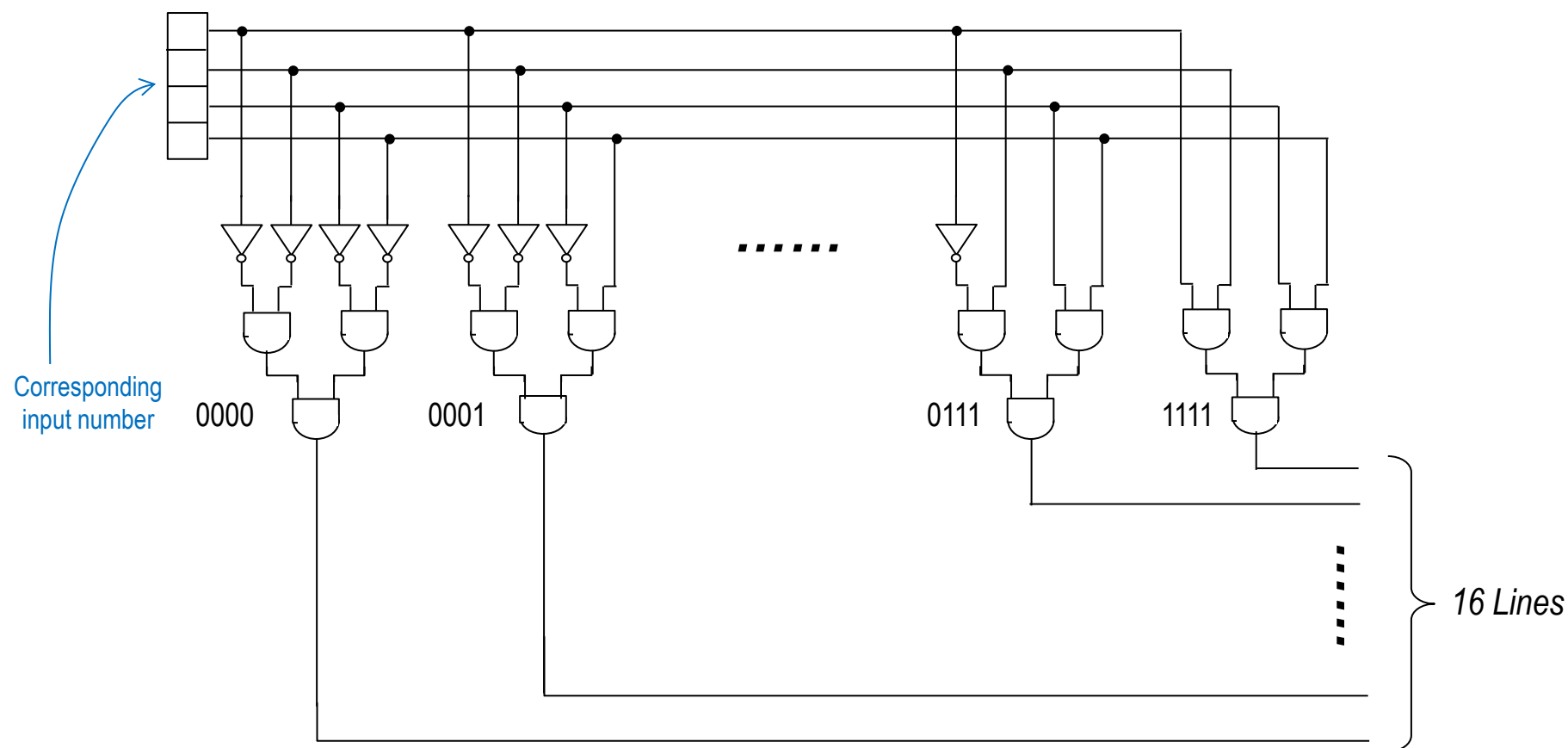
Example: 4-bit number controlling/selecting 16 lines



n-bit Input Controlling/Selecting 2^n Different Actions

4-bit Decode

4-bit binary number

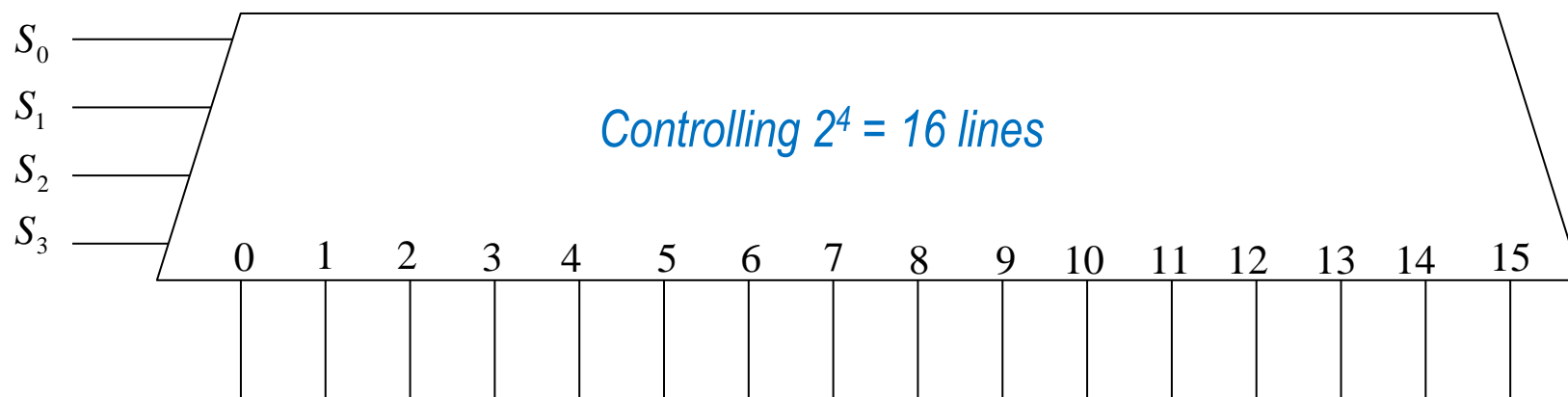


This is how machine(computer) uses binary numbers to perform different actions!

n-bit Input Controlling/Selecting 2ⁿ Different Actions

4-bit Decode


4-bit binary number: 1011

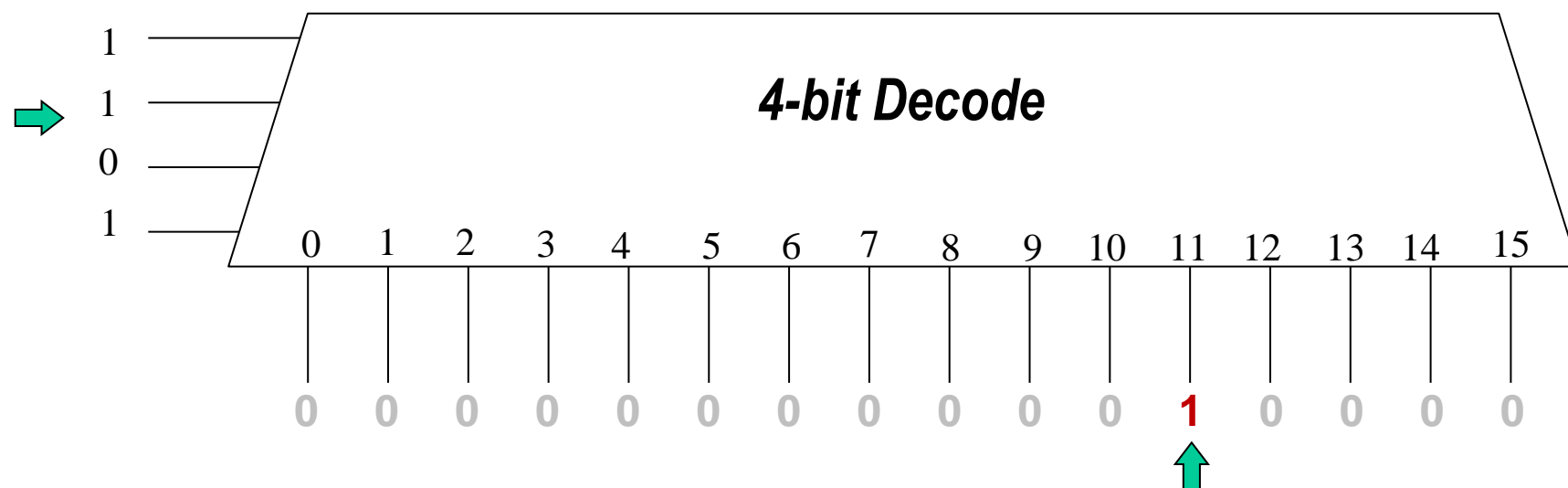

*A 4-bit binary number selects a single line (out of the 16 lines) to be “HIGH”.
(The rest all remain “LOW”)*

4-bit Input Controlling/Selecting 2^4 Different Actions

4-bit binary number 0111

 


A 4-bit binary number selects a single line (out of the 16 lines) to be "HIGH".
(The rest all remain "LOW")

Does This Look Familiar ?




3-bit decoder





 


NAND Gate :

AND gate + NOT gate

 

NAND gate

     


Truth Table

$$P = \overline{A \cdot B}$$


| Input A | Input B | Output P |
|---------|---------|----------|
| 0 | 0 | 1 |
| 1 | 0 | 1 |
| 0 | 1 | 1 |
| 1 | 1 | 0 |

$$\left\{ \begin{array}{l} \overline{0 \cdot 0} = \overline{0} = 1 \\ \overline{1 \cdot 0} = \overline{0} = 1 \\ \overline{0 \cdot 1} = \overline{0} = 1 \\ \overline{1 \cdot 1} = \overline{1} = 0 \end{array} \right.$$

CMOS Logic

 



NAND Gate

 

| A | B | Out |
|---|---|-----|
| 0 | 0 | 1 |
| 1 | 0 | 1 |
| 0 | 1 | 1 |
| 1 | 1 | 0 |

CMOS Logic



NAND Gate

 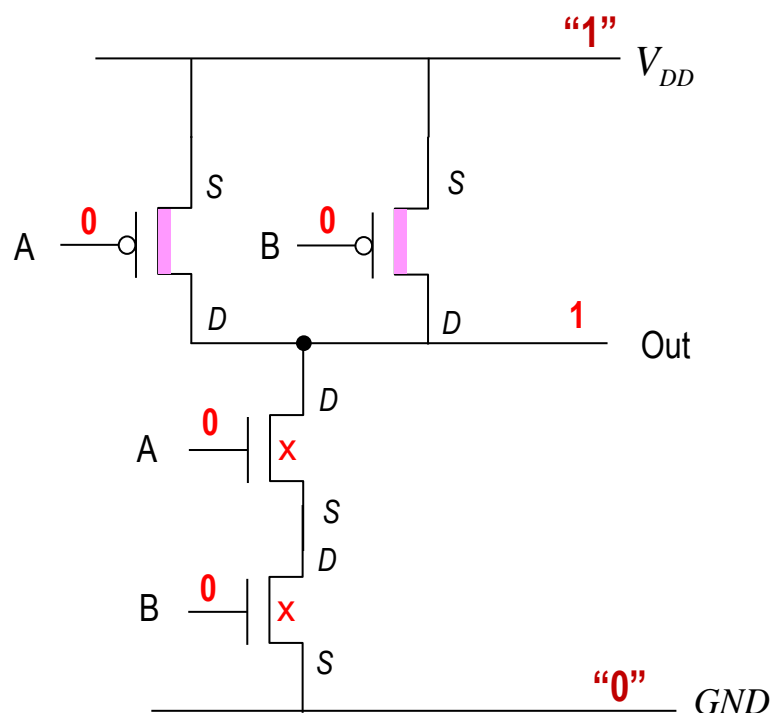

| A | B | Out |
|---|---|-----|
| 0 | 0 | 1 |
| 1 | 0 | 1 |
| 0 | 1 | 1 |
| 1 | 1 | 0 |

CMOS Logic



NAND Gate

 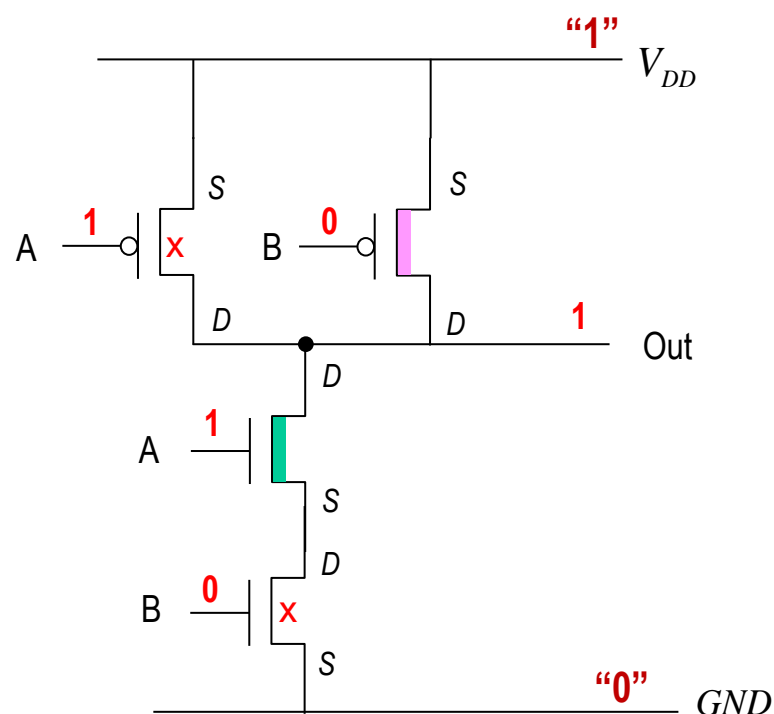

| A | B | Out |
|---|---|-----|
| 0 | 0 | 1 |
| 1 | 0 | 1 |
| 0 | 1 | 1 |
| 1 | 1 | 0 |

CMOS Logic



NAND Gate

 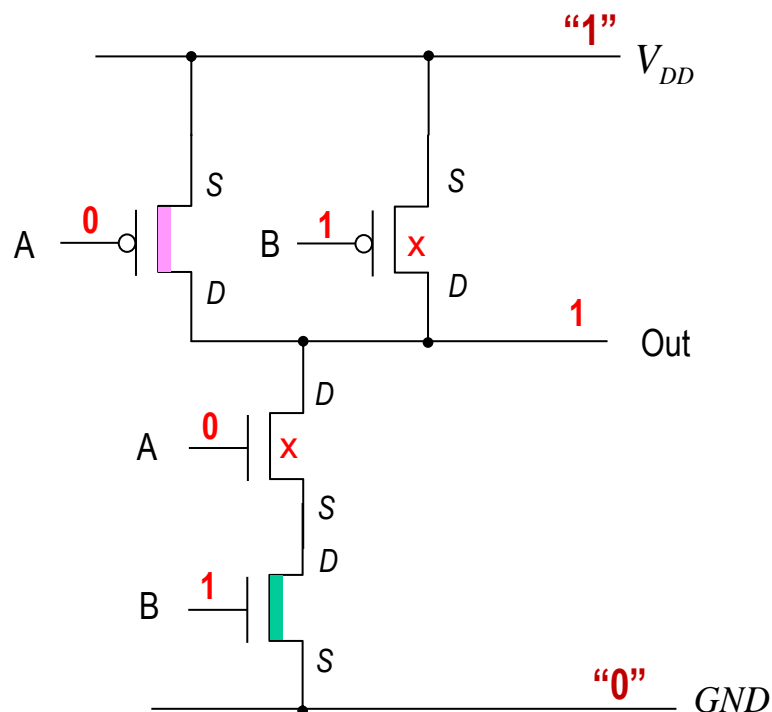

| A | B | Out |
|---|---|-----|
| 0 | 0 | 1 |
| 1 | 0 | 1 |
| 0 | 1 | 1 |
| 1 | 1 | 0 |






CMOS Logic

NAND Gate

 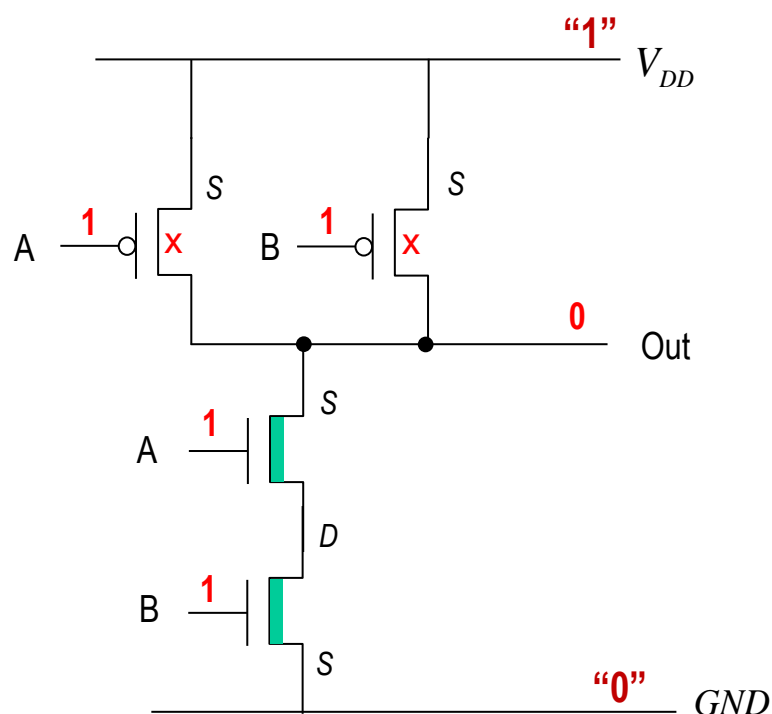

| A | B | Out |
|---|---|-----|
| 0 | 0 | 1 |
| 1 | 0 | 1 |
| 0 | 1 | 1 |
| 1 | 1 | 0 |

OR Gate

     






Truth Table

$$C = A + B$$

| Input A | Input B | Output C |
|---------|---------|----------|
| 0 | 0 | 0 |
| 1 | 0 | 1 |
| 0 | 1 | 1 |
| 1 | 1 | 1 |

$$\left\{ \begin{array}{l} 0 + 0 = 0 \\ 1 + 0 = 1 \\ 0 + 1 = 1 \\ 1 + 1 = 1 \end{array} \right.$$

Exclusive OR Gate: XOR

     

Truth Table

$$C = A \oplus B$$

| Input A | Input B | Output C |
|---------|---------|----------|
| 0 | 0 | 0 |
| 0 | 1 | 1 |
| 1 | 0 | 1 |
| 1 | 1 | 0 |


$$\left\{ \begin{array}{l} 0 \oplus 0 = 0 \\ 1 \oplus 0 = 1 \\ 0 \oplus 1 = 1 \\ 1 \oplus 1 = 0 \end{array} \right.$$

Computing Using Logic Gates: Addition

Adding Binary Numbers for the Rightmost Digit (No Input Carry)

$$\begin{array}{r|rrrrr}
 A & & & & & \\
 + B & & & & & \\
 \hline
 & 0 & 1 & 0 & 1 & \\
 & + 0 & + 0 & + 1 & + 1 & \\
 \hline
 & 0 & 1 & 1 & 0 &
 \end{array}$$

Half Adder (no input carry)

 


| A | B | Sum | Carry |
|---|---|-----|-------|
| 0 | 0 | 0 | 0 |
| 0 | 1 | 1 | 0 |
| 1 | 0 | 1 | 0 |
| 1 | 1 | 0 | 1 |

Computing Using Logic Gates: Addition

Adding Binary Numbers for the Rightmost Digit (No Input Carry)

$$\begin{array}{r}
 A \\
 + B \\
 \hline
 \end{array}
 \quad
 \begin{array}{r}
 0 \\
 + 0 \\
 \hline
 0
 \end{array}
 \quad
 \begin{array}{r}
 1 \\
 + 0 \\
 \hline
 1
 \end{array}
 \quad
 \begin{array}{r}
 0 \\
 + 1 \\
 \hline
 1
 \end{array}
 \quad
 \begin{array}{r}
 1 \\
 + 1 \\
 \hline
 10
 \end{array}$$

Half Adder (no input carry)

 


| A | B | Sum | Carry |
|---|---|-----|-------|
| 0 | 0 | 0 | 0 |
| 0 | 1 | 1 | 0 |
| 1 | 0 | 1 | 0 |
| 1 | 1 | 0 | 1 |

Computing Using Logic Gates: Addition

Adding Binary Numbers for the Rightmost Digit (No Input Carry)

$$\begin{array}{r}
 A \\
 + B \\
 \hline
 \end{array}
 \quad
 \begin{array}{r}
 0 \\
 + 0 \\
 \hline
 0
 \end{array}
 \quad
 \begin{array}{r}
 1 \\
 + 0 \\
 \hline
 1
 \end{array}
 \quad
 \begin{array}{r}
 0 \\
 + 1 \\
 \hline
 1
 \end{array}
 \quad
 \begin{array}{r}
 1 \\
 + 1 \\
 \hline
 10
 \end{array}$$

Half Adder (no input carry)

 


| A | B | Sum | Carry |
|---|---|-----|-------|
| 0 | 0 | 0 | 0 |
| 0 | 1 | 1 | 0 |
| 1 | 0 | 1 | 0 |
| 1 | 1 | 0 | 1 |

Computing Using Logic Gates: Addition

Adding Binary Numbers for the Rightmost Digit (No Input Carry)

$$\begin{array}{r}
 A \\
 + B \\
 \hline
 \end{array}
 \quad
 \begin{array}{r}
 0 \\
 + 0 \\
 \hline
 0
 \end{array}
 \quad
 \begin{array}{r}
 1 \\
 + 0 \\
 \hline
 1
 \end{array}
 \quad
 \begin{array}{r}
 0 \\
 + 1 \\
 \hline
 1
 \end{array}
 \quad
 \begin{array}{r}
 1 \\
 + 1 \\
 \hline
 10
 \end{array}$$

Half Adder (no input carry)

 


| A | B | Sum | Carry |
|---|---|-----|-------|
| 0 | 0 | 0 | 0 |
| 0 | 1 | 1 | 0 |
| 1 | 0 | 1 | 0 |
| 1 | 1 | 0 | 1 |

Computing Using Logic Gates: Addition

Adding Binary Numbers for the Rightmost Digit (No Input Carry)

$$\begin{array}{r}
 A \\
 + B \\
 \hline
 \end{array}
 \quad
 \begin{array}{r}
 0 \\
 + 0 \\
 \hline
 0
 \end{array}
 \quad
 \begin{array}{r}
 1 \\
 + 0 \\
 \hline
 1
 \end{array}
 \quad
 \begin{array}{r}
 0 \\
 + 1 \\
 \hline
 1
 \end{array}
 \quad
 \begin{array}{r}
 1 \\
 + 1 \\
 \hline
 10
 \end{array}$$

Half Adder (no input carry)

 


| A | B | Sum | Carry |
|---|---|-----|-------|
| 0 | 0 | 0 | 0 |
| 0 | 1 | 1 | 0 |
| 1 | 0 | 1 | 0 |
| 1 | 1 | 0 | 1 |

Addition


Addition with input carry:

$$\begin{array}{r} 0 \\ + 0_1 \\ \hline 1 \end{array} \quad \begin{array}{r} 1 \\ + 1_0_1 \\ \hline 0 \end{array} \quad \begin{array}{r} 0 \\ + 1_1_1 \\ \hline 0 \end{array} \quad \begin{array}{r} 1 \\ + 1_1_1 \\ \hline 1 \end{array}$$


Full Adder (with input carry)

 

Full Adder

 

8-bit Adder

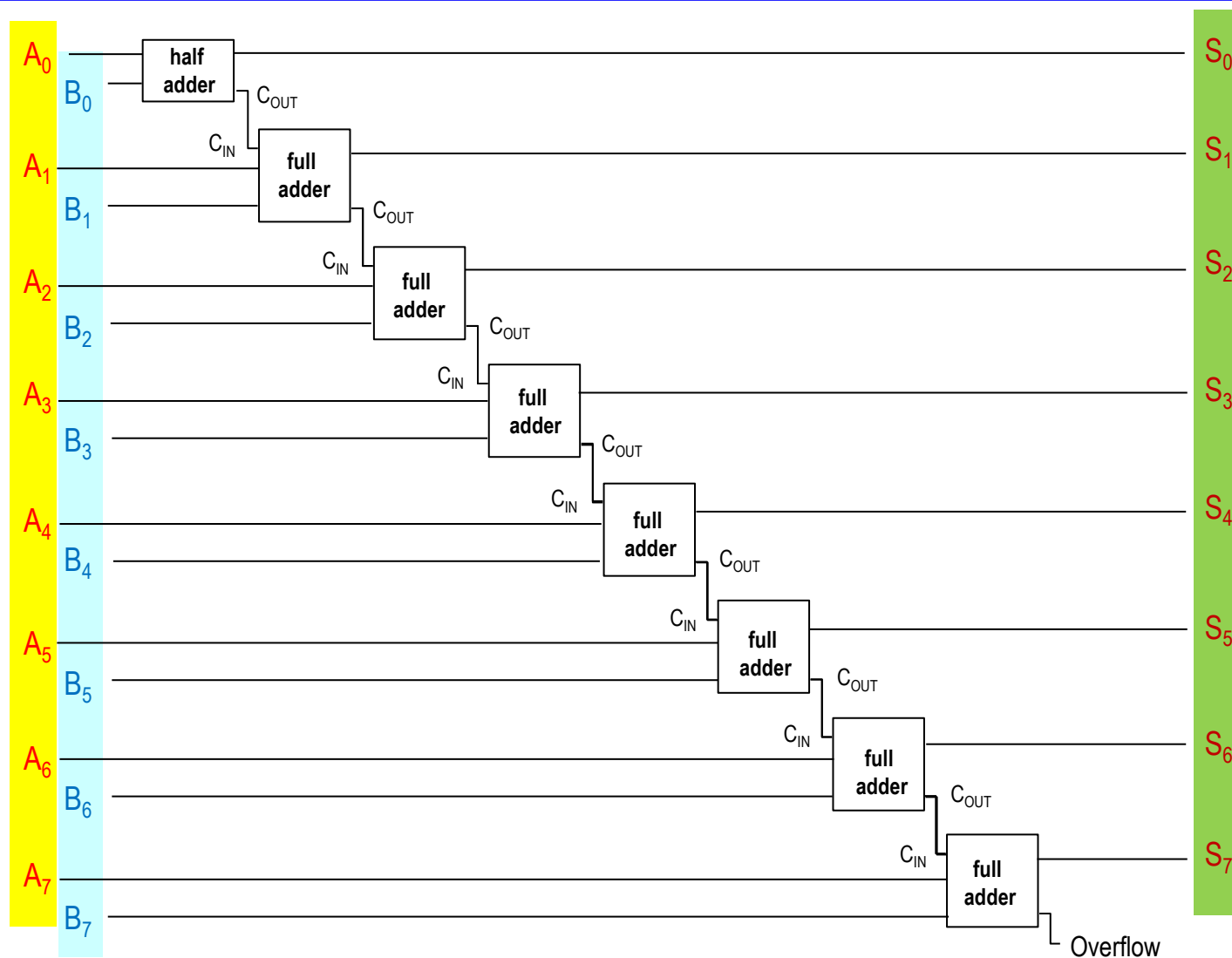


Deriving 2s Complement Signed Representation

(Kesden draws here during lecture)

Boolean Algebra


Rules

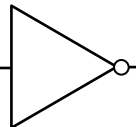
 $X \rightarrow Z = \bar{X}$

$$\begin{cases} X = 1 \Rightarrow Z = 0 \\ X = 0 \Rightarrow Z = 1 \end{cases}$$

X and \bar{X} are complements

$$\bar{\bar{X}} = X$$

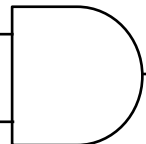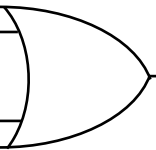

 $X, Y \rightarrow Z = X \cdot Y$

$$\begin{cases} 0 \cdot 0 = 0 \\ 1 \cdot 0 = 0 \\ 0 \cdot 1 = 0 \\ 1 \cdot 1 = 1 \end{cases}$$

$$0 \cdot X = 0$$

$$X \cdot \bar{X} = 0$$

$$1 \cdot X = X$$


 $X, Y \rightarrow Z = X + Y$

$$\begin{cases} 0 + 0 = 0 \\ 1 + 0 = 1 \\ 0 + 1 = 1 \\ 1 + 1 = 1 \end{cases}$$


$$0 + X = X$$

$$1 + X = 1$$

$$X + \bar{X} = 1$$


$$X + Y = Y + X$$

Boolean Algebra

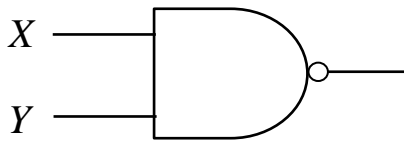


$$Z = \overline{X \cdot Y}$$
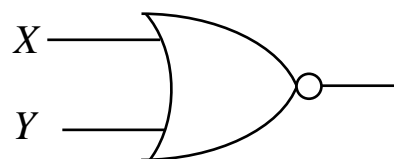
$$\left\{ \begin{array}{l} \overline{0 \cdot 0} = \overline{0} = 1 \\ \overline{1 \cdot 0} = \overline{0} = 1 \\ \overline{0 \cdot 1} = \overline{0} = 1 \\ \overline{1 \cdot 1} = \overline{1} = 0 \end{array} \right.$$



$$Z = \overline{X + Y}$$
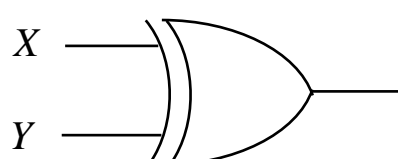
$$\left\{ \begin{array}{l} \overline{0 + 0} = \overline{0} = 1 \\ \overline{1 + 0} = \overline{1} = 0 \\ \overline{0 + 1} = \overline{1} = 0 \\ \overline{1 + 1} = \overline{1} = 0 \end{array} \right.$$



$$Z = X \oplus Y$$

$$\left\{ \begin{array}{l} 0 \oplus 0 = 0 \\ 1 \oplus 0 = 1 \\ 0 \oplus 1 = 1 \\ 1 \oplus 1 = 0 \end{array} \right.$$

Rules for Boolean Algebra

1. $0 + X = X$

2. $1 + X = 1$

3. $X + X = X$

4. $X + \bar{X} = 1$

5. $0 \cdot X = 0$

6. $1 \cdot X = X$

7. $X \cdot X = X$

8. $X \cdot \bar{X} = 0$

9. $\bar{\bar{X}} = X$

10. $X + Y = Y + X$

Commutative Law

11. $X \cdot Y = Y \cdot X$

Commutative Law

12. $X + (Y + Z) = (X + Y) + Z$



13. $X \cdot (Y \cdot Z) = (X \cdot Y) \cdot Z$

14. $X \cdot (Y + Z) = X \cdot Y + X \cdot Z$

Distributive Law

15. $X + X \cdot Z = X$

Absorption Law

  

De Morgan's Laws

$$\overline{(X + Y)} = \bar{X} \cdot \bar{Y}$$

$$\overline{(X \cdot Y)} = \bar{X} + \bar{Y}$$

- Any logic function can be implemented using only **OR** and **NOT** gates.
- Any logic function can be implemented using only **AND** and **NOT** gates.

Boolean Algebra Example

Fail-Safe Autopilot Logic

Prior to takeoff or landing maneuver, a commercial aircraft requires the following check:

2 of the possible 3 pilots must be available: the pilot, the copilot and the autopilot

Set Logic Variables:

X – State of the pilot: 1= Present, 0=Absent

Y – State of the copilot: 1= Present, 0=Absent

Z – State of the autopilot: 1= Functioning, 0=Not Functioning

Logic function corresponding to “System Ready” is

$$f = X \text{ and } Y$$

$$f = X \cdot Y + X \cdot Z + Y \cdot Z$$

$$f = 1 : \text{System Ready}; \quad f = 0 : \text{System Not Ready}$$

Boolean Algebra Example

Fail-Safe Autopilot Logic

Positive check

$$f = X \cdot Y + X \cdot Z + Y \cdot Z \quad \text{sum-of-product}$$

System Not Ready Condition:

$$\overline{f} = \overline{X \cdot Y + X \cdot Z + Y \cdot Z}$$

$$= \overline{(X \cdot Y)} \cdot \overline{(X \cdot Z)} \cdot \overline{(Y \cdot Z)}$$

$$\overline{(X + Y)} = \overline{X} \cdot \overline{Y}$$

$$= (\overline{X} + \overline{Y}) \cdot (\overline{X} + \overline{Z}) \cdot (\overline{Y} + \overline{Z})$$


$$\overline{(X \cdot Y)} = \overline{X} + \overline{Y}$$

$$\overline{f} = (\overline{X} + \overline{Y}) \cdot (\overline{X} + \overline{Z}) \cdot (\overline{Y} + \overline{Z})$$


Maintaining State w/ Logic Gates: Latches that Never Forget

Logic Gates + Feedback:

OR gate


 


OR gate + feedback

 


Logic Gates + Feedback:

Making a Memory

  


It stores/memorizes “1”

Store “1”

 


After a “1” is stored, the state cannot be changed.

Unless the power is turned-off to reset.





 


RS Latches: Latches that can Reset

NOR Gate

 


=

     

Truth Table


| Input A | Input B | Output P |
|---------|---------|----------|
| 0 | 0 | 1 |
| 0 | 1 | 0 |
| 1 | 0 | 0 |
| 1 | 1 | 0 |

Latch with NOR Gates

 


Latch with NOR Gates:

Set Q to "1"

 


Latch with NOR Gates:

Set Q to "1"

 


Latch with NOR Gates:

Set Q to "1"

 


Latch with NOR Gates:

$Q = "1"$ is "Latched"

 


Latch with NOR Gates

Reset Q to "0"

 


Latch with NOR Gates:

Reset Q to "0"

 


Latch with NOR Gates:

Reset Q to "0"

 


Latch with NOR Gates:

Reset Q to "0"

 


Latch with NOR Gates:

$Q = "0"$ is "Latched"

 


RS Latch

 


S — Set
R — Reset



| R | S | Q |
|---|---|-----------|
| 0 | 0 | no change |
| 0 | 1 | 1 |
| 1 | 0 | 0 |
| 1 | 1 | illegal |

 




RS Latch

 


Using Latch to Memorize/Store “Request”

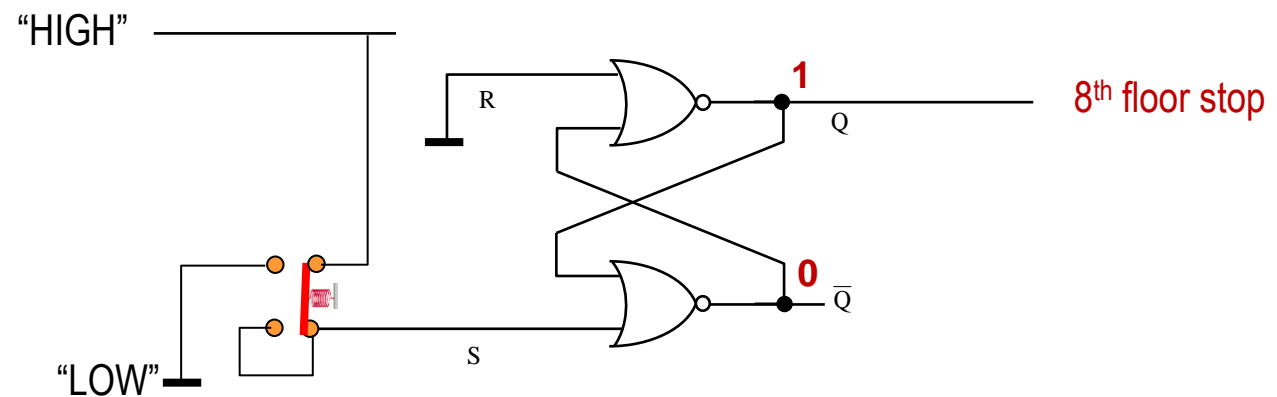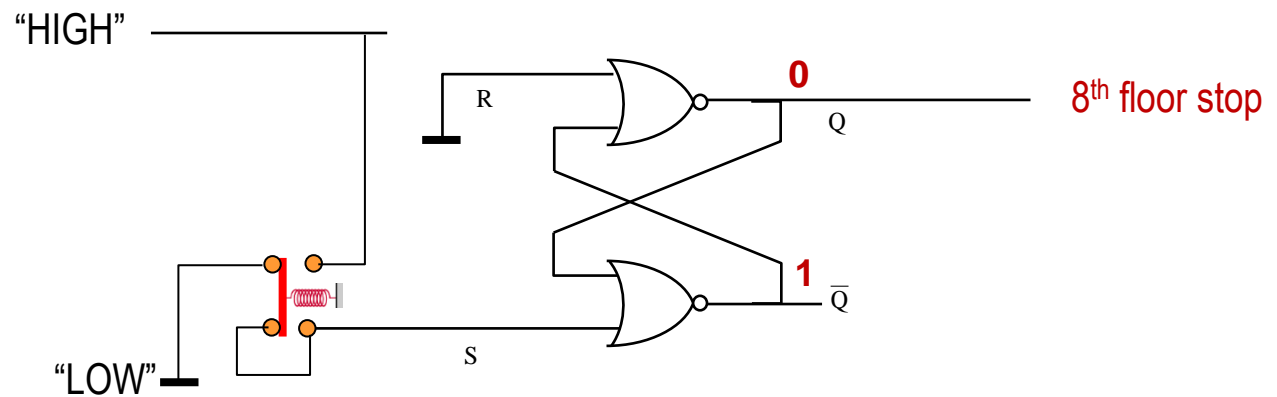

The Use of Latch

  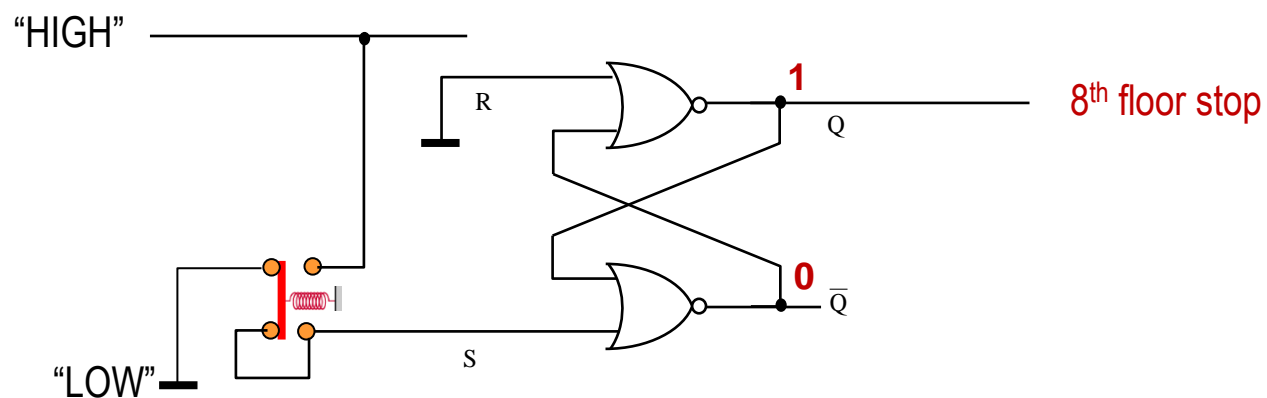



Gated SR Latch (with Enable)

 

E — Enable







D Latches and 1-Bit Memories

D-Latch

  

| E | D | Q |
|---|---|----------------|
| 0 | 0 | Latched/Stored |
| 0 | 1 | Latched/Stored |
| 1 | 0 | 0 |
| 1 | 1 | 1 |

1-Bit Memory: D-Latch

      

$Q = "1"$

$Q = "0"$

Coming Attractions

- ***Next class: Building Memory***
- ***Monday: Building a Computer!***